

1. Specification





- BCD to Excess-5 converter
- Transforms BCD code for the decimal digits to Excess-5 code for the decimal digits
- BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- Excess-5 code words for digits 0 through 9: 4-bit patterns consisting of 5 (binary 0101) added to each BCD code word

2. Formulation

- BCD variables = ABCD
- Excess-5 variables = WXYZ
- Don't cares = 1010-1111

BCD	Excess-5
0000	0101
0001	0110
0010	0111
0011	1000
0100	1001
0101	1010
0110	1011
0111	1100
1000	1101
1001	1110

3. Optimization

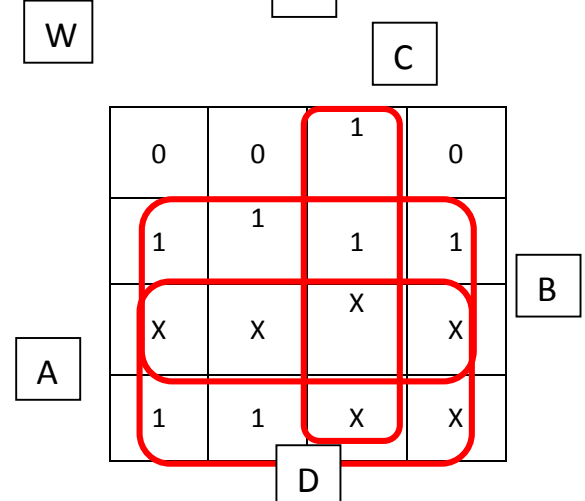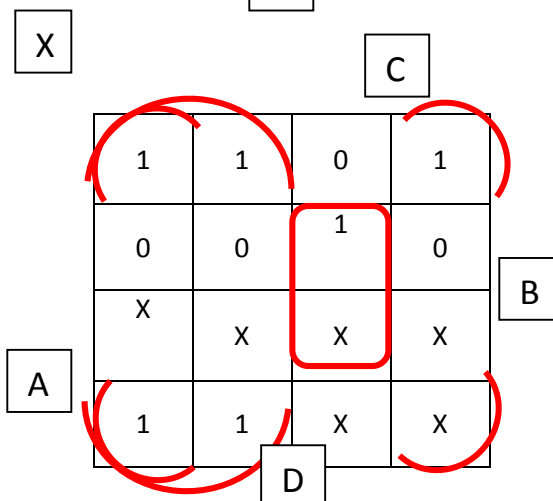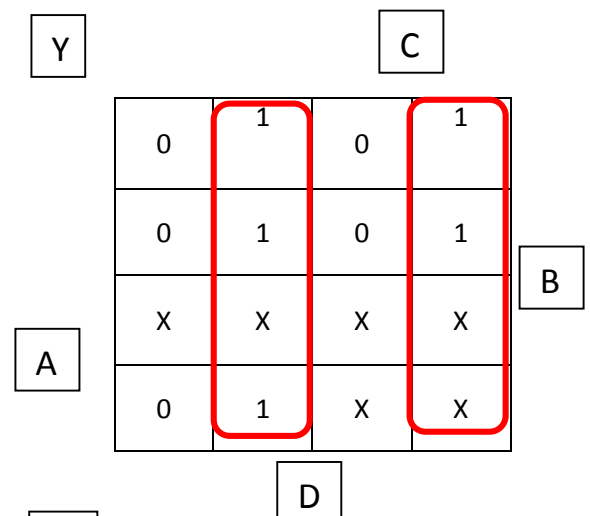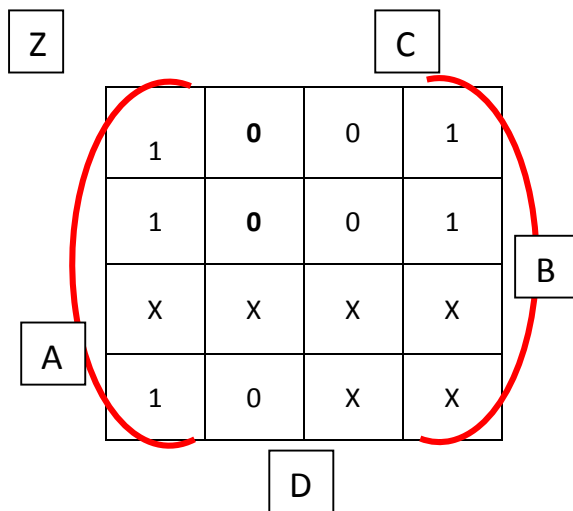

Maka dari K-Maps tadi bisa didapatkan assignment untuk W, X, Y, Z


$$W = A + B + CD$$

$$X = B'C' + B'D' + BDC$$

$$Y = DC' + D'C$$

$$Z = D'$$

4. Mapping Procedures

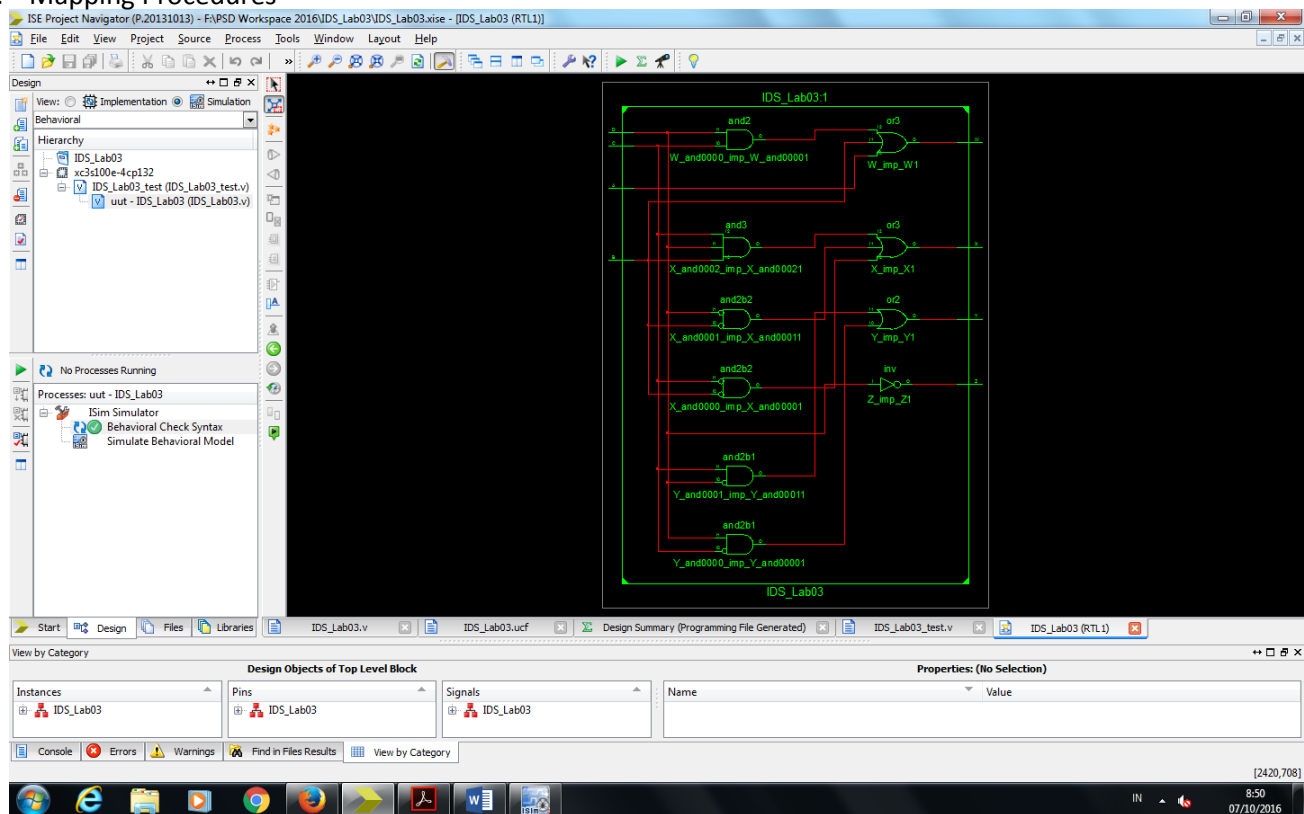

5. Verification

